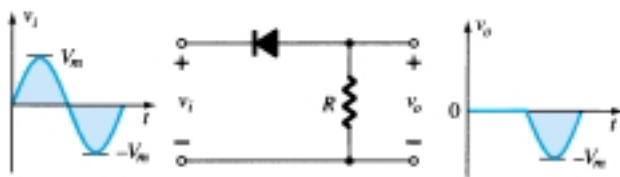





Simple Series Clippers (Ideal Diodes)



POSITIVE





NEGATIVE

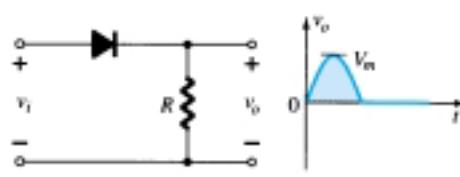

Biased Series Clippers (Ideal Diodes)

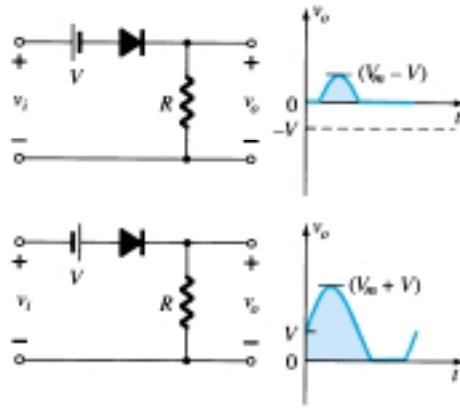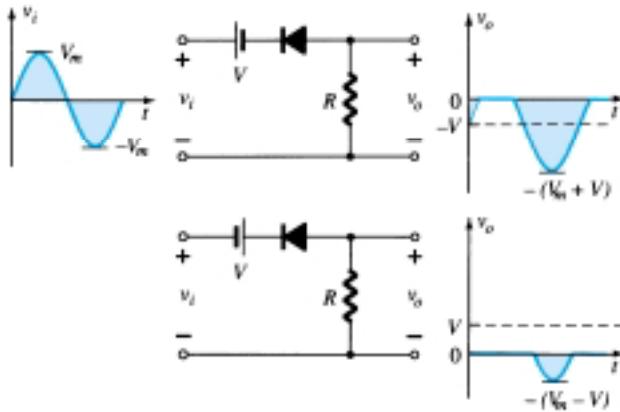

Simple Parallel Clippers (Ideal Diodes)

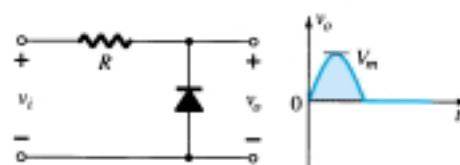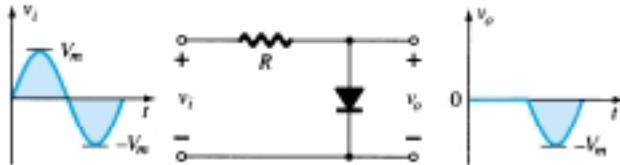

Biased Parallel Clippers (Ideal Diodes)

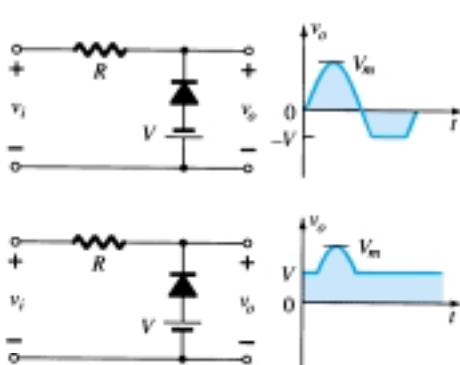
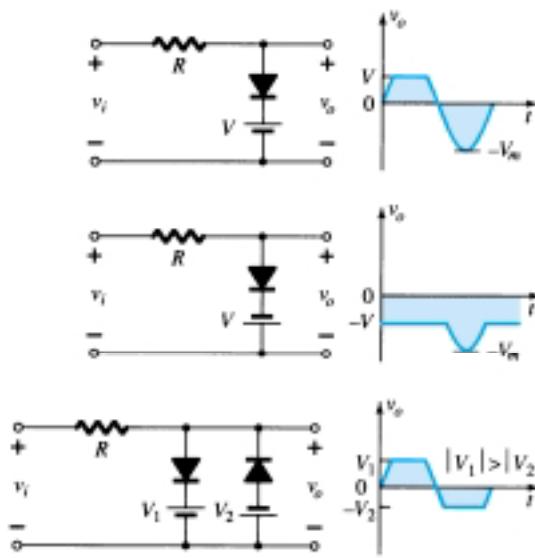


Figure 2.91 Clipping circuits.