

B1


④ I_D, V_R

$$I_D = \left[\frac{30 - 0.7}{2.2} \right]$$


$I_D = 13.32 \text{ m. ampere}$

$$V_R = I_D R_D = 29.3 \text{ Volt}$$


OR, $V_R = 30 - 0.7 = 29.3 \text{ VOLT}$

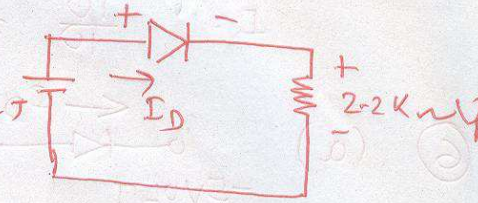

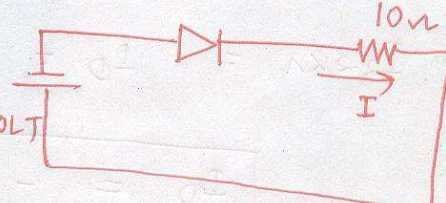⑤ (a) DIODE is REVERSE BIAS. $I = 0$ CIRCUIT IS OPEN CIRCUITED.




(b)

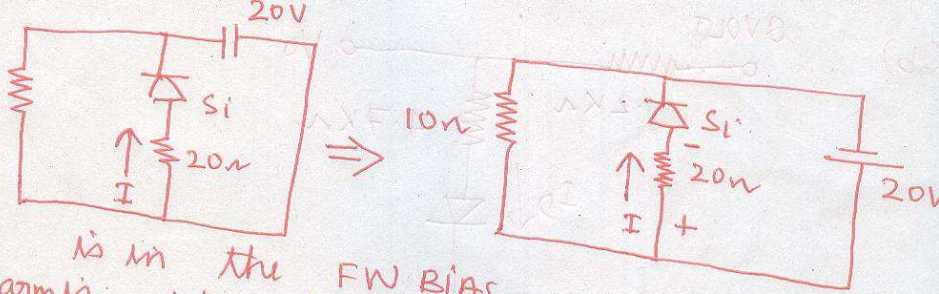

DIODE is in the FW BIAS in the parallel to the power source.

$$I = \frac{20 - 0.7}{20} = 0.965 \text{ mA}$$

(c)

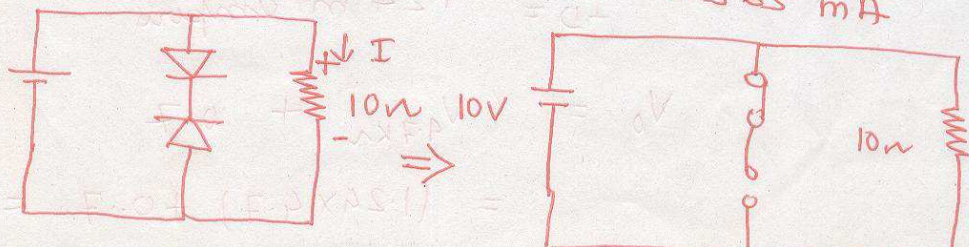

⑥ (a)

$I = \frac{10}{10} = 1 \text{ ampere}$

$V_o = -5 - 0.7 = -5.7 \text{ VOLT}$

$V_o = 5 - 0.7 = 4.3 \text{ VOLT}$

Since diode is reverse with the resistance then

$I_{2.2k\Omega} = I_D = \frac{V_o}{2.2} = \frac{-4.3}{2.2}$

$I_D = -1.955 \text{ m.ampere}$

(b)

$I_D = \left[\frac{8 - 0.7}{1.2 + 4.7} \right] = \frac{7.3}{5.9}$

$I_D = 1.24 \text{ m.ampere}$

$V_o = V_{4.7k\Omega} + 0.7$

$= (1.24 \times 4.7) + 0.7 = 6.53 \text{ VOLT}$

⑦ (a)

20VOLT Si Ge 2kΩ 2kΩ V_0

$$I = \frac{20 - 0.7 - 0.3}{2 + 2} = \frac{19}{4} \text{ m.ampere}$$

$$V_0 = IR = \frac{19}{2} \text{ m.ampere VOLT}$$

(b)

10VOLT 12kΩ Si 4.7kΩ V_0

$$I = \frac{10 - 0.7 + 2}{12 + 4.7} = \frac{11.3}{16.7} = 0.676 \text{ m.ampere}$$

$$V_{4.7k\Omega} = [1.915 \times 4.7] = 9 \text{ VOLT}$$

$$V_0 = 9 - 2 = 7 \text{ VOLT}$$

⑧ (a)

10mA 2.2kΩ 1.2kΩ V_0 2.2kΩ 22VOLT 1.2kΩ V_0

$$I_D = \left[\frac{22 - 0.7}{2.2 + 1.2} \right] = \frac{21.3}{3.4} \times 10^{-3}$$

$$I_D = 6.26 \text{ m.ampere}$$

$$V_0 = 6.62 \times 1.2$$

$$V_0 = 7.51 \text{ VOLT}$$

(b)

$$I = \left[\frac{20 + 5 - 0.7}{6.8} \right] = \left[\frac{24.3}{6.8} \right]$$

$$I = 3.57 \text{ m.ampere}$$

$$20 = (6.8 \times 3.57) + V_0$$

$$V_0 = 20 - 24.27$$

$$V_0 = -4.27 \text{ VOLT}$$

$$V_{02} = 0.3 \text{ VOLT}$$

$$V_{01} = 12 - 0.7 = 11.3 \text{ VOLT}$$

B3

$V_{01} = -10 + 0.3 + 0.7$
 $V_{01} = -9 \text{ VOLT}$

$I = \frac{-10 + 1}{3.3 + 1.2} = \frac{-9}{4.5}$
 $I = -2 \text{ m. ampere}$

$V_{02} = (-2) \times 3.3$
 $V_{02} = -6.6 \text{ VOLT}$

⑩



$V_0 = 20 - 0.7$
 $V_0 = 19.3 \text{ VOLT}$

$I = \left[\frac{19.3}{4.7} \right] = 4.106 \text{ m. ampere}$

$V_0 = 4.106 \times 4.7 = 19.3 \text{ VOLT}$

$I_D = m \left(\frac{I}{2} \right) = \frac{0V}{2} = 2.054 \text{ m. ampere}$

(b)

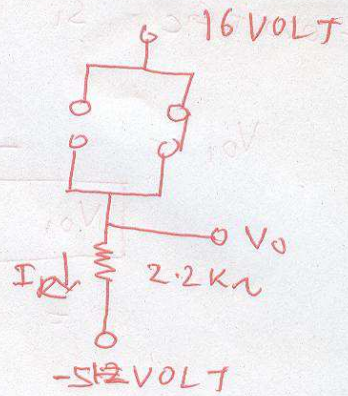
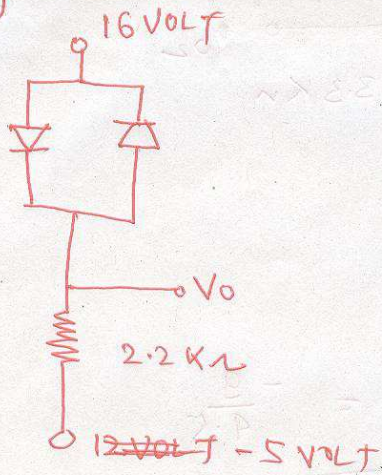


$$V_o = 16 - 0.7 = 15.3 \text{ VOLT}$$

$$I_R = \left[\frac{20 - 0.7 + 5}{2.2} \right] = 0.77 \text{ m. ampere}$$

$$I_D = I_R = 0.77 \text{ m. ampere}$$

(11) (a)

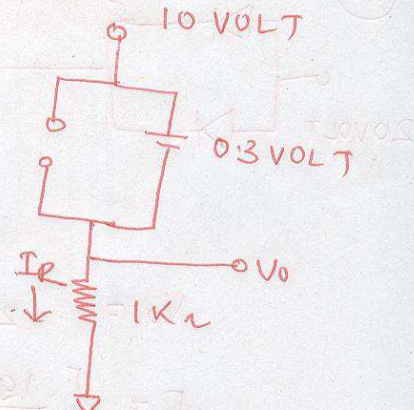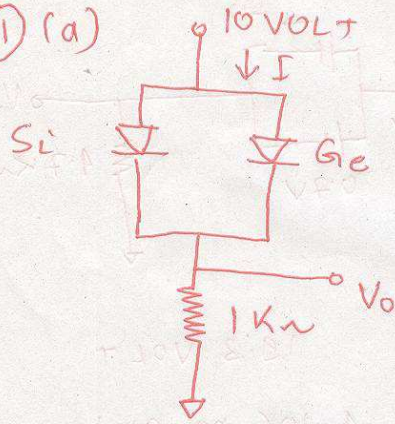

$$V_o = 10 - 0.3 = 9.7 \text{ VOLT}$$

$$I_R = \frac{V_o}{1k\Omega} = 9.7 \text{ m. ampere}$$

(b) B4

$$V_0 = 16 - 0.7 - 0.7$$

$$V_0 = 14.6 \text{ VOLT}$$

$$I_R = \left[\frac{14.6 - 12}{4.7} \right] = 0.553 \text{ m. ampere}$$

(12)

$$V_{01} = 0.7 \text{ VOLT}$$

$$V_{02} = 0.3 \text{ VOLT}$$

$$I_{1k\Omega} = \left[\frac{20 - 0.7}{1} \right] = 19.3 \text{ m. ampere}$$

$$I_{0.47k\Omega} = \left[\frac{0.7 - 0.3}{0.47} \right] =$$

$I_{0.47} = 0.051 \text{ m.ampere}$
 $I = 19.3 - 0.051$
 $I = 18.45 \text{ mampere}$

13

$V_0 = \frac{10 - 0.7}{1 + 2} \times 2 = \frac{2}{3} \times 9.3$
 $V_0 = 6.2 \text{ VOLT}$
 $I_2 = \frac{V_0}{2} = 3.1 \text{ m.ampere}$
 $I_D = \frac{I_2}{2} = 1.55 \text{ m.ampere}$