

Mathematical Solution of the problems  
of Assignment - 4

01

10.37 From the problem

$$Z_0 = 75 \Omega$$

$$f = 150 \times 10^6 \text{ Hz}$$

$$\alpha = 0.06 \text{ Np/m}$$

$$v_p = 2.8 \times 10^8 \text{ m/Ae}$$

Since the line is distortionless line then

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$$

$$\alpha = \sqrt{RG}$$

$$v_p = \frac{1}{\sqrt{LC}}$$

$$\alpha Z_0 = R$$

$$\Rightarrow R = 0.06 \times 75 = 4.5 \Omega/\text{m}$$

$$\sqrt{RG} = \alpha$$

$$\Rightarrow G = \frac{\alpha^2}{R} = \frac{36 \times 10^{-4}}{4.5}$$

$$= 8 \times 10^{-4} \text{ S/m}$$

Now,

$$v_p Z_0 = \frac{1}{C} = 75 \times 2.8 \times 10^8$$

$$C = \frac{10^{-8}}{75 \times 2.8}$$

$$= 4.76 \times 10^{-11} \text{ F/m}$$

$$L = \frac{Z_0}{v_p} = \frac{75}{2.8 \times 10^8} = 2.678 \times 10^{-7} \text{ H/m} \quad (02)$$

10.20

From the problem, it is given  
 when the line  $Z_0 = 40 \Omega$  is behave like as short  
 circuit then,

$$Z_{sc} = jZ_0 \tan \beta L$$

$$\Rightarrow j73 = j40 \tan \beta L$$

$$\Rightarrow \tan \beta L = \frac{73}{40} = 1.738$$

$$\Rightarrow \tan \beta L = \tan 60$$

$$\Rightarrow \beta L = \frac{\pi}{3}$$

$$\Rightarrow \frac{2\pi}{\lambda} \times L = \frac{\pi}{3}$$

$$\Rightarrow L = \lambda/6$$

when the line is behave like as open  
 circuit then,

$$Z_{oc} = -jZ_0 \cot \beta L$$

$$\Rightarrow j73 = -j40 \cot \beta L$$

$$\Rightarrow \cot \beta L = -1.738$$

$$\Rightarrow \cot \beta L = \cot \left( \frac{2\pi}{3} \right) \cot \left( \frac{5\pi}{6} \right)$$

$$\Rightarrow \beta L = \frac{5\pi}{6}$$

$$\Rightarrow \frac{2\pi}{\lambda} \times L = \frac{5\pi}{6}$$

$$\Rightarrow l = \frac{5\lambda}{12}$$

(03)

10.30

This transmission line is connected as shown in the figure. The input impedance of the last <sup>(third)</sup> waveguide is the load impedance of the second waveguide. Now for the third waveguide

$$Z_{03} = 75 \Omega$$

$$Z_{L3} = (60 - 40j) \Omega$$

$$l_3 = (3\lambda/4)$$

For any waveguide, the input impedance is calculated by

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

For third waveguide

$$\begin{aligned} \tan \beta l_3 &= \tan \left( \frac{2\pi}{\lambda} \times \frac{3\lambda}{4} \right) \\ &= \tan \left( \frac{3\pi}{2} \right) = \infty \end{aligned}$$

So,

$$\begin{aligned} Z_{m_3} &= Z_{02} \left[ \frac{Z_{L3} + j Z_{03} \tan \beta l_3}{Z_{03} + j Z_{L3} \tan \beta l_3} \right] \\ &= Z_{03} \left[ \frac{\frac{Z_{L3}}{\tan \beta l_3} + j Z_{03}}{\frac{Z_{03}}{\tan \beta l_3} + j Z_{L3}} \right] \end{aligned}$$

04

$$\Rightarrow Z_{m3} = Z_{03} \times \frac{Z_{03}}{Z_{L3}}$$

$$\Rightarrow Z_{m3} = \frac{Z_{03}^2}{Z_{L3}}$$

For the 2<sup>nd</sup> waveguide

$$Z_{L2} = Z_{m3}$$

$$L_2 = \lambda/2$$

$$\tan \beta L_2 = \tan\left(\frac{2\pi}{\lambda} \times \frac{\lambda}{2}\right) = \tan \pi$$

$$Z_{m2} = Z_{02} \left[ \frac{Z_{L2} + j Z_{02} \tan \beta L_2}{Z_{02} + j Z_{L2} \tan \beta L_2} \right]$$

$$= Z_{02} \times \frac{Z_{L2}}{Z_{02}} = Z_{L2}$$

$$\text{So } Z_{m2} = Z_{L2} = \left[ \frac{Z_{03}^2}{Z_{L3}} \right]$$

For the first waveguide

$$Z_{L1} = Z_{m2} = \frac{Z_{03}^2}{Z_{L3}}$$

$$L_1 = \lambda/4$$

$$\text{Now } \tan \beta L_1 = \tan\left(\frac{2\pi}{\lambda} \times \frac{\lambda}{4}\right)$$

$$= \tan\left(\frac{\pi}{2}\right) = \infty$$

$$Z_{m1} = Z_{01} \left[ \frac{Z_{L1} + j Z_{01} \tan \beta L_1}{Z_{01} + j Z_{L1} \tan \beta L_1} \right]$$

$$= Z_0 \left[ \frac{\frac{Z_L}{\tan \beta L} + j Z_0}{\frac{Z_0}{\tan \beta L} + j Z_L} \right] \quad (05)$$

$$= Z_0 \left[ \frac{Z_0}{Z_L} \right] = \frac{Z_0^2}{Z_L}$$

$$= \frac{Z_0^2}{Z_0} \times Z_L$$

$$= \frac{50 \times 50}{75 \times 75} \times (60 - j40)$$

$$= \frac{4}{9} (60 - j40) \approx$$

(10.32) From the problem  
 $Z_0 = 75 \Omega$

$$Z_L = [120 + j80] \Omega$$

Reflection coefficient

$$\Gamma = \left[ \frac{Z_L - Z_0}{Z_L + Z_0} \right] = \left[ \frac{120 + j80 - 75}{120 + j80 + 75} \right]$$

$$= 0.435 \angle 38.34$$

$$VSWR = \left[ \frac{1 + |\Gamma|}{1 - |\Gamma|} \right] = \left[ \frac{1 + 0.435}{1 - 0.435} \right]$$

$$= 2.54$$

The load is mismatched when

$$\frac{38^\circ}{72^\circ} \rightarrow \frac{38}{72} = 0.528$$

10.35 From the problem



06

$$Z_0 = 50 \Omega$$

$$L = 4.2 \text{ mt}$$

$$f = 300 \text{ MHz} = 3 \times 10^8 \text{ Hz}$$
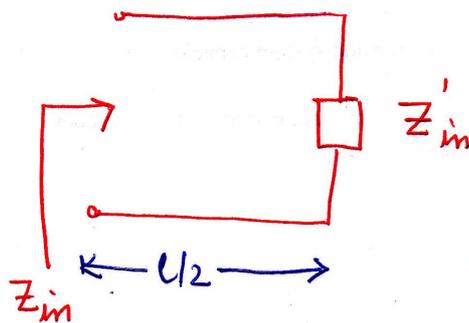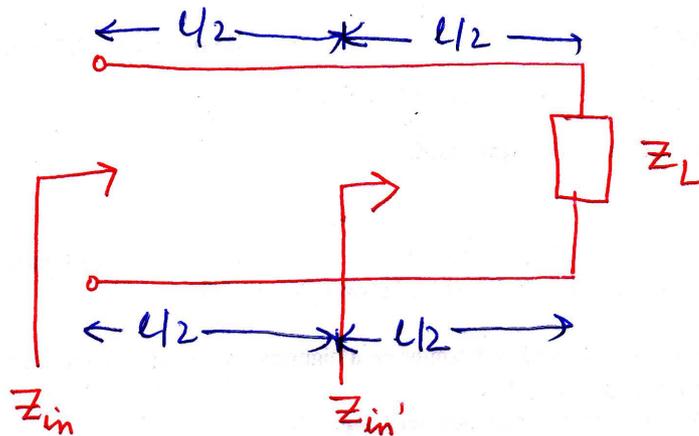
$$v_p = 0.8c = 2.4 \times 10^8 \text{ mt}$$



From the figure, it is clear that input impedance of a waveguide work as the load impedance of the another series connected waveguide.

$$Z_L = Z_{in}' = (80 - 60j) \Omega$$

$$\tan(\beta l) = \tan\left(\frac{2\pi}{\lambda} \times 2.1\right)$$

$$= \tan\left(\frac{2\pi f}{c} \times 2.1\right)$$

(07)

$$= \tan\left[\frac{2\pi \times 3 \times 10^8}{2.4 \times 10^8} \times 2.1\right]$$

$$= \tan\left[\frac{4.2\pi}{0.8}\right] = \tan\left(\frac{21\pi}{4}\right)$$

$$= \tan\left(5\pi + \frac{\pi}{4}\right) = \tan\frac{\pi}{4} = 1$$

Input impedance of the waveguide

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta L}{Z_0 + jZ_L \tan \beta L} \right]$$

$$= 50 \left[ \frac{80 - 60j + 50j}{50 + j80 + 60} \right]$$

$$= [21.6 - j20.2] \Omega$$

$$\Gamma = \left[ \frac{Z_L - Z_0}{Z_L + Z_0} \right] = \left[ \frac{80 - 60j - 50}{80 - 60j + 50} \right]$$

$$= 0.4685 \angle -38.66$$

$$\theta_L = -38.66$$

$$\theta_L' = \theta_L + 2n(\pi/4)$$

$$= 51.34$$

Reflection coefficient

(08)

$$\Gamma = 0.485 \angle 51.34$$

10.39

$$VSWR = \left[ \frac{V_{max}}{V_{min}} \right] = \frac{0.8}{0.5} = 1.6$$

$$\frac{\lambda}{2} = [19 - 9.5] = 9.5 \text{ c.m.}$$

$$\lambda = 19 \text{ c.m.}$$

$$f = \frac{c}{\lambda} = \frac{3 \times 10^8}{19 \times 10^{-2}} = 1.58 \text{ GHz}$$

$$L = 19 - 14 = 5 \text{ c.m.}$$

$$= \frac{5\lambda}{19} = 189.4$$

$$Z_L = Z_0 Z_L = 50 [1.59 + j0.14]$$

$$= [79.5 + j7] \Omega$$

$$|\Gamma| = \left[ \frac{VSWR - 1}{VSWR + 1} \right] = \frac{1.6 - 1}{1.6 + 1}$$

$$= \frac{0.6}{2.6} = 0.231$$

10.45

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - 50}{30 + 50}$$

$$= -\frac{20}{80} = -\frac{1}{4}$$

$$\Gamma_g = \left[ \frac{Z_g - Z_0}{Z_g + Z_0} \right] = \left[ \frac{75 - 50}{75 + 50} \right] \quad (0.9)$$

$$= \frac{25}{125} = \frac{1}{5}$$

$$t_1 = \frac{L}{c} = \frac{600}{3 \times 10^8} = 2 \mu\text{s}$$

$$V_0 = \left[ \frac{Z_0}{Z_0 + Z_g} \right] V_g = \frac{50 \times 30}{125} = \frac{10 \times 30}{50}$$

$$= 12 \text{ Volt}$$

$$V_\infty = \left[ \frac{Z_L}{Z_L + Z_0} \right] \times V_g = \frac{30 \times 30}{75 + 30}$$

$$= 8.571 \text{ Volt}$$

$$I_0 = \frac{V_0}{Z_0} = \frac{12}{50} = 240 \text{ mA}$$

$$I_\infty = \frac{V_\infty}{Z_L} = \frac{30}{105} = 285.7 \text{ mA}$$

(10.48)

$$V_\infty = \frac{Z_L}{Z_L + Z_g} \times V_g$$

$$= \left[ \frac{100 \times 200}{100 + 50} \right] = 133.33 \text{ V}$$

$$I_\infty = \frac{V_\infty}{Z_L} = 133.33$$

10.57

$$L = \left[ \frac{Z_0}{\nu_p} \right] = \frac{Z_0 \sqrt{\epsilon}}{c}$$

10

$$= \frac{60 \sqrt{5}}{3 \times 10^8} = 1 \mu\text{H/m}$$

$$C = \frac{1}{Z_0 \nu_p} = \frac{\sqrt{\epsilon}}{Z_0 c}$$

$$= \frac{\sqrt{5}}{60 \times 3 \times 10^8} = 0.1242 \text{ nF/m}$$

